
10 - RF Oscillators

The information in this work has been obtained from sources believed to be reliable. The author does not guarantee the accuracy or completeness of any information presented herein, and shall not be responsible for any errors, omissions or damages as a result of the use of this information.

April 2012

© 2006 by Fabian Kung Wai Lee

1

Main References

- [1]* D.M. Pozar, "Microwave engineering", 2nd Edition, 1998 John-Wiley & Sons.
- [2] J. Millman, C. C. Halkias, "Integrated electronics", 1972, McGraw-Hill.
- [3] R. Ludwig, P. Bretchko, "RF circuit design - theory and applications", 2000 Prentice-Hall.
- [4] B. Razavi, "RF microelectronics", 1998 Prentice-Hall, TK6560.
- [5] J. R. Smith, "Modern communication circuits", 1998 McGraw-Hill.
- [6] P. H. Young, "Electronics communication techniques", 5th edition, 2004 Prentice-Hall.
- [7] Gilmore R., Besser L., "Practical RF circuit design for modern wireless systems", Vol. 1 & 2, 2003, Artech House.
- [8] Ogata K., "Modern control engineering", 4th edition, 2005, Prentice-Hall.

April 2012

© 2006 by Fabian Kung Wai Lee

2

Agenda

- Positive feedback oscillator concepts.
- Negative resistance oscillator concepts (typically employed for RF oscillator).
- Equivalence between positive feedback and negative resistance oscillator theory.
- Oscillator start-up requirement and transient.
- Oscillator design - Making an amplifier circuit unstable.
- Constant $|\Gamma_1|$ circle.
- Fixed frequency oscillator design.
- Voltage-controlled oscillator design.

1.0 Oscillation Concepts


Introduction

- Oscillators are a class of circuits with 1 terminal or port, which produce a periodic electrical output upon power up.
- Most of us would have encountered oscillator circuits while studying for our basic electronics classes.
- Oscillators can be classified into two types: (A) Relaxation and (B) Harmonic oscillators.
- Relaxation oscillators (also called astable multivibrator), is a class of circuits with two unstable states. The circuit switches back-and-forth between these states. The output is generally square waves.
- Harmonic oscillators are capable of producing near sinusoidal output, and is based on positive feedback approach.
- Here we will focus on **Harmonic Oscillators** for RF systems. Harmonic oscillators are used as this class of circuits are capable of producing stable sinusoidal waveform with low phase noise.

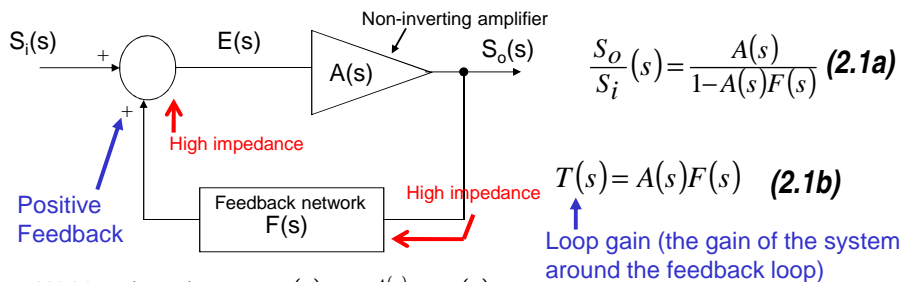2.0 Overview of Feedback Oscillators

Classical Positive Feedback Perspective on Oscillator (1)

- Consider the classical feedback system with non-inverting amplifier,
- Assuming the feedback network and amplifier do not load each other, we can write the closed-loop transfer function as:



- Writing (2.1a) as: $S_o(s) = \frac{A(s)}{1-A(s)F(s)} S_i(s)$
- We see that we could get non-zero output at S_o , with $S_i = 0$, provided $1-A(s)F(s) = 0$. Thus the system oscillates!

April 2012

© 2006 by Fabian Kung Wai Lee

7

Classical Positive Feedback Perspective on Oscillator (1)

- The condition for sustained oscillation, and for oscillation to startup from positive feedback perspective can be summarized as:

For sustained oscillation $1 - A(s)F(s) = 0$ ← Barkhausen Criterion (2.2a)

For oscillation to startup $|A(s)F(s)| > 1$ $\arg(A(s)F(s)) = 0$ (2.2b)

- Take note that the oscillator is a non-linear circuit, initially upon power up, the condition of (2.2b) will prevail. As the magnitudes of voltages and currents in the circuit increase, the amplifier in the oscillator begins to saturate, reducing the gain, until the loop gain $A(s)F(s)$ becomes one.
- A steady-state condition is reached when $A(s)F(s) = 1$.

Note that this is a very simplistic view of oscillators. In reality oscillators are non-linear systems. The steady-state oscillatory condition corresponds to what is called a **Limit Cycle**. See texts on non-linear dynamical systems.


April 2012

© 2006 by Fabian Kung Wai Lee

8

Classical Positive Feedback Perspective on Oscillator (2)

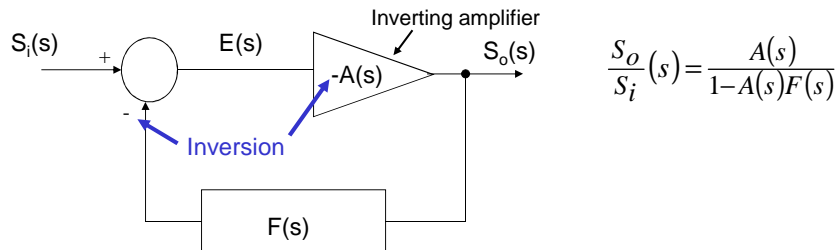- Positive feedback system can also be achieved with inverting amplifier:



- To prevent multiple simultaneous oscillation, the Barkhausen criterion (2.2a) should only be fulfilled at one frequency.
- Usually the amplifier **A** is wideband, and it is the function of the feedback network **F(s)** to 'select' the oscillation frequency, thus the feedback network is usually made of reactive components, such as inductors and capacitors.


April 2012

© 2006 by Fabian Kung Wai Lee

9

Classical Positive Feedback Perspective on Oscillator (3)

- In general the feedback network $F(s)$ can be implemented as a Pi or T network, in the form of a transformer, or a hybrid of these.
- Consider the Pi network with all reactive elements. A simple analysis in [2] and [3] shows that to fulfill (2.2a), the reactance X_1 , X_2 and X_3 need to meet the following condition:

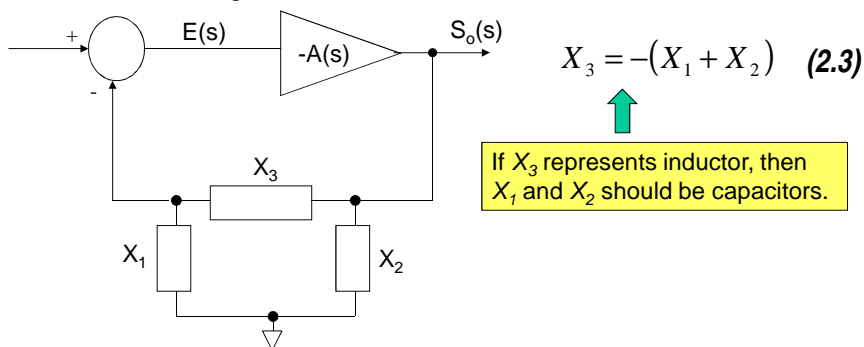


April 2012

© 2006 by Fabian Kung Wai Lee

10

Classical Feedback Oscillators

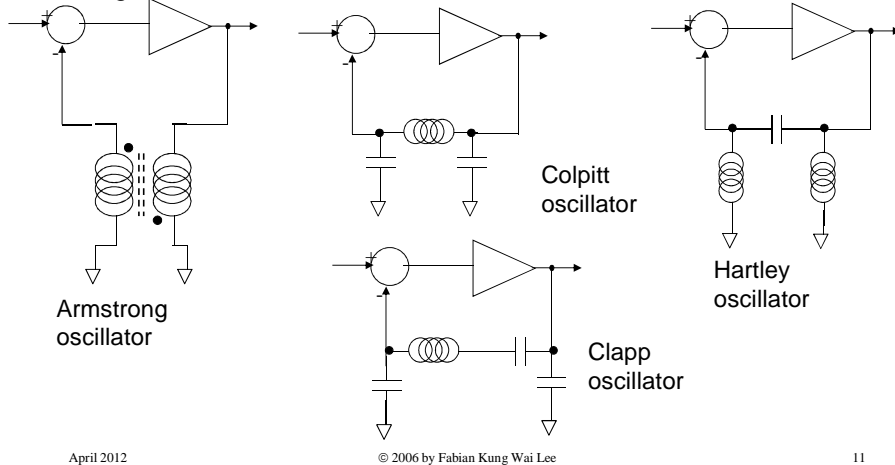
- The following are examples of oscillators, based on the original circuit using vacuum tubes.



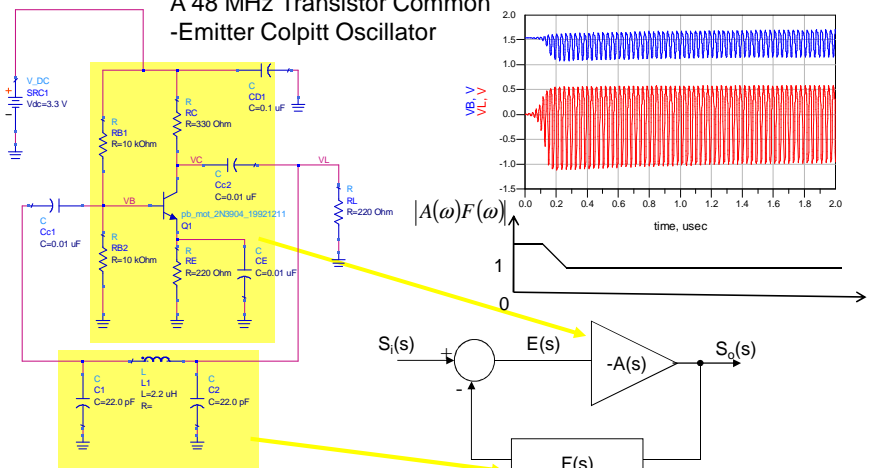Example of Tuned Feedback Oscillator (1)






A 48 MHz Transistor Common-Emitter Colpitt Oscillator



Example of Tuned Feedback Oscillator (2)

Extra

A 27 MHz Transistor Common-Base Colpitt Oscillator

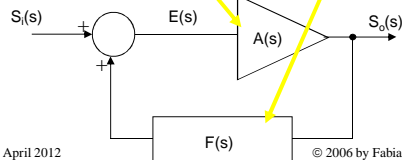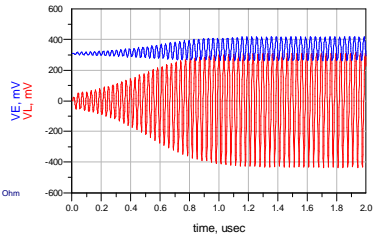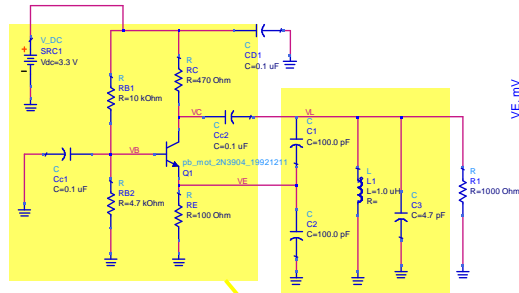

April 2012



© 2006 by Fabian Kung Wai Lee

13

Example of Tuned Feedback Oscillator (3)

Extra

A 16 MHz Transistor Common-Emitter Crystal Oscillator

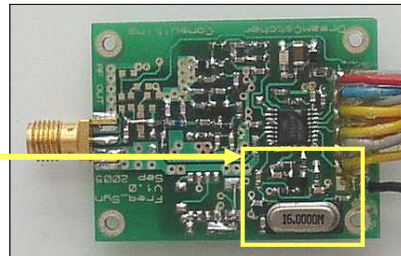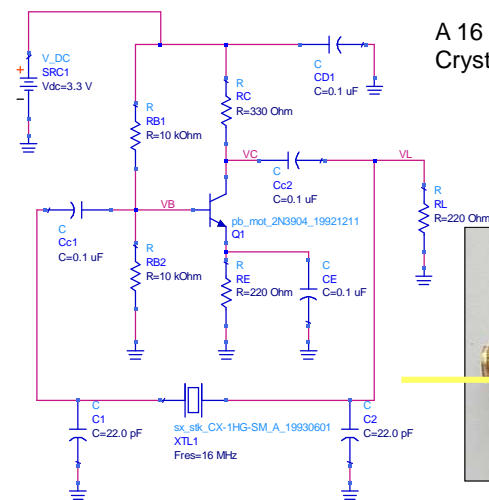

April 2012

© 2006 by Fabian Kung Wai Lee

14

Limitation of Feedback Oscillator

- At high frequency, the assumption that the amplifier and feedback network do not load each other is not valid. In general the amplifier's input impedance decreases with frequency, and its output impedance is not zero. Thus the actual loop gain is not $A(s)F(s)$ and equation (2.2) breakdowns.
- Determining the loop gain of the feedback oscillator is cumbersome at high frequency. Moreover there could be multiple feedback paths due to parasitic inductance and capacitance.
- It can be difficult to distinguish between the amplifier and the feedback paths, owing to the coupling between components and conductive structures on the printed circuit board (PCB) or substrate.
- Generally it is difficult to physically implement a feedback oscillator once the operating frequency is higher than 500MHz.

3.0 Negative Resistance Oscillators

Introduction (1)

- An alternative approach is needed to get a circuit to oscillate reliably.
- We can view an **oscillator as an amplifier that produces an output when there is no input**.
- Thus it is an unstable amplifier that becomes an oscillator!
- For example let's consider a conditionally stable amplifier.
- Here instead of choosing load or source impedance in the stable regions of the Smith Chart, we purposely choose the load or source impedance in the **unstable impedance regions**. This will result in either $|\Gamma_1| > 1$ or $|\Gamma_2| > 1$.
- The resulting amplifier circuit will be called the **Destabilized Amplifier**.
- As seen in Chapter 7, having a reflection coefficient magnitude for Γ_1 or Γ_2 greater than one implies the corresponding port resistance R_1 or R_2 is negative, hence the name for this type of oscillator.


April 2012

© 2006 by Fabian Kung Wai Lee

17

Introduction (2)

- For instance by choosing the load impedance Z_L at the unstable region, we could ensure that $|\Gamma_1| > 1$. We then choose the source impedance properly so that $|\Gamma_1 \Gamma_s| > 1$ and oscillation will start up (refer back to Chapter 7 on stability theory).
- Once oscillation starts, **an oscillating voltage will appear at both the input and output ports of a 2-port network**. So it does not matter whether we enforce $|\Gamma_1 \Gamma_s| > 1$ or $|\Gamma_2 \Gamma_L| > 1$, enforcing either one will cause oscillation to occur (It can be shown later that when $|\Gamma_1 \Gamma_s| > 1$ at the input port, $|\Gamma_2 \Gamma_L| > 1$ at the output port and vice versa).
- The key to fixed frequency oscillator design is ensuring that the criteria $|\Gamma_1 \Gamma_s| > 1$ only happens at **one frequency (or a range of intended frequencies)**, so that no simultaneous oscillations occur at other frequencies.

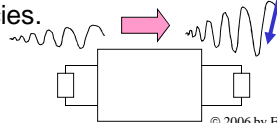

April 2012


© 2006 by Fabian Kung Wai Lee

18

Recap - Wave Propagation Stability Perspective (1)

Extra

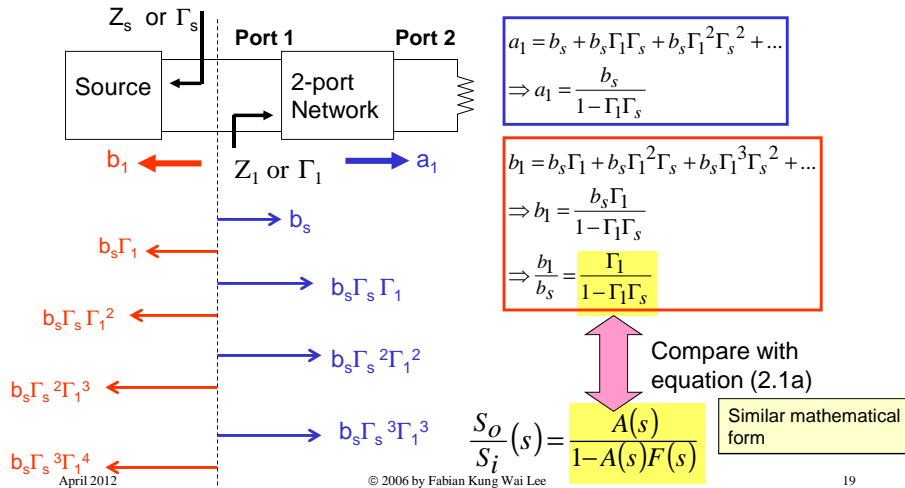- From our discussion of stability from wave propagation in Chapter 7...




Recap - Wave Propagation Stability Perspective (2)

Extra

- We see that the infinite series that constitute the steady-state incident (a_1) and reflected (b_1) waves at Port 1 will only converge provided $|\Gamma_s \Gamma_1| < 1$.
- These sinusoidal waves correspond to the voltage and current at the Port 1. If the waves are unbounded it means the corresponding sinusoidal voltage and current at the Port 1 will grow larger as time progresses, indicating oscillation start-up condition.
- Therefore oscillation will occur when $|\Gamma_s \Gamma_1| > 1$.
- Similar argument can be applied to port 2 since the signals at Port 1 and 2 are related to each other in a two-port network, and we see that the condition for oscillation at Port 2 is $|\Gamma_L \Gamma_2| > 1$.

Oscillation from Negative Resistance Perspective (1)

- Generally it is more useful to work with impedance (or admittance) when designing actual circuit.
- Furthermore for practical purpose the transmission lines connecting Z_L and Z_s to the destabilized amplifier are considered very short (length $\rightarrow 0$).
- In this case the impedance Z_o is ambiguous (since there is no transmission line).
- To avoid this ambiguity, let us ignore the transmission line and examine the condition for oscillation phenomena in terms of terminal impedance.

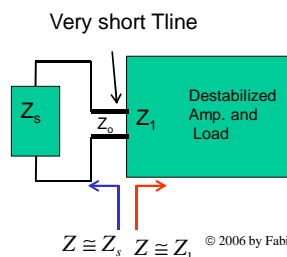


April 2012

© 2006 by Fabian Kung Wai Lee

21

Oscillation from Negative Resistance Perspective (2)

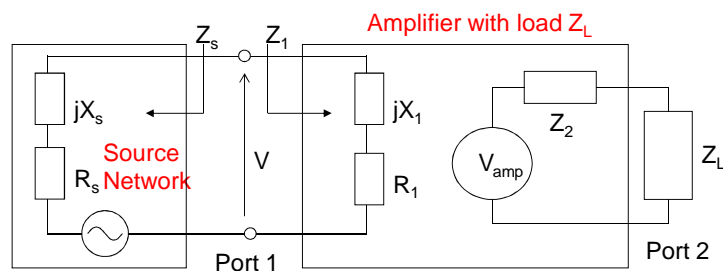- We consider Port 1 as shown, with the source network and input of the amplifier being modeled by impedance or series networks.



- Using circuit theory the voltage at Port 1 can be written as:

$$V = \frac{R_1 + jX_1}{R_1 + R_s + j(X_1 + X_s)} \cdot V_s = \frac{Z_1}{Z_s + Z_1} V_s \quad (3.1)$$


April 2012

© 2006 by Fabian Kung Wai Lee

22

Oscillation from Negative Resistance Perspective (3)

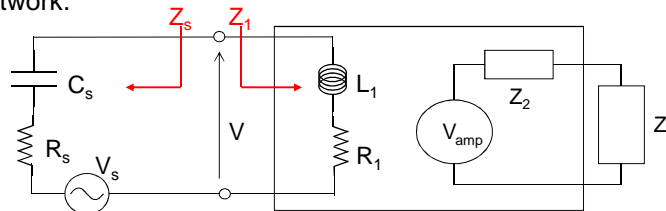- Furthermore we assume the source network Z_s is a series RC network and the equivalent circuit looking into the amplifier Port 1 is a series RL network.



- Using Laplace Transform, (3.1) is written as:

$$V(s) = \frac{R_1 + sL_1}{R_1 + R_s + sL_1 + \frac{1}{sC_s}} \cdot V_s(s) \quad (3.2a)$$

$$\text{where } s = \sigma + j\omega \quad (3.2b)$$

April 2012

© 2006 by Fabian Kung Wai Lee

23

Oscillation from Negative Resistance Perspective (4)

- The expression for $V(s)$ can be written in the “standard” form according to **Control Theory [8]**:

$$\frac{V}{V_s}(s) = \frac{1}{L_1} \cdot \frac{s(R_1 + sL_1)}{s^2 + s\left(\frac{R_1 + R_s}{L_1}\right) + \frac{1}{L_1 C_s}} = \frac{sC_s(R_1 + sL_1)\omega_n^2}{s^2 + 2\omega_n\delta s + \omega_n^2} \quad (3.3a)$$

$$\text{where } \delta = \frac{R_1 + R_s}{2\sqrt{L_1/C_s}} = \text{Damping Factor} \quad \omega_n = \frac{1}{\sqrt{L_1 C_s}} = \text{Natural Frequency} \quad (3.3b)$$

- The transfer function $V(s)/V_s(s)$ is thus a 2nd order system with two poles p_1, p_2 given by:

$$p_{1,2} = -\delta\omega_n \pm \omega_n\sqrt{\delta^2 - 1} \quad (3.4)$$

- Observe that if $(R_1 + R_s) < 0$ the damping factor δ is negative. This is true if R_1 is negative, and $|R_1| > R_s$.
- R_1 can be made negative by modifying the amplifier circuit (e.g. adding local positive feedback), producing the sum $R_1 + R_s < 0$.


April 2012

© 2006 by Fabian Kung Wai Lee

24

Oscillation from Negative Resistance Perspective (5)

- Assuming $|\delta| < 1$ (under-damped), the poles as in (3.4) will be complex and exist at the right-hand side of the complex plane.
- From Control Theory such a system is unstable. Any small perturbation will result in a oscillating signal with frequency $\omega_n \sqrt{\delta^2 - 1}$ that grows exponentially.

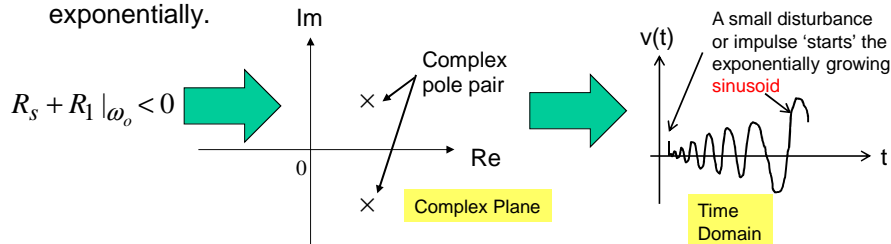

- Usually a transient or noise signal from the environment will contain a small component at the oscillation frequency. This forms the 'seed' in which the oscillation builds up.

April 2012

© 2006 by Fabian Kung Wai Lee

25

Oscillation from Negative Resistance Perspective (6)

- When the signal amplitude builds up, nonlinear effects such as transistor saturation and cut-off will occur, this limits the β of the transistor and finally limits the amplitude of the oscillating signal.
- The effect of decreasing β of the transistor is a reduction in the magnitude of R_1 (remember R_1 is negative). Thus the damping factor δ will approach 0, since $R_s + R_1 \rightarrow 0$.
- Steady-state sinusoidal oscillation is achieved when $\delta = 0$, or equivalently the poles become

$$p_{1,2}|_{\delta=0} = \pm j\omega_n$$

- The steady-state oscillation frequency ω_o corresponds to ω_n ,

$$\begin{aligned} \omega_n^2 &= \frac{1}{L_1 C_s} \Rightarrow \omega_n L_1 = \frac{1}{\omega_n C_s} \Rightarrow X_1 = |X_s| \\ \Rightarrow X_1 + X_s|_{\omega_o} &= 0 \end{aligned}$$

April 2012

© 2006 by Fabian Kung Wai Lee

26

Oscillation from Negative Resistance Perspective (7)

- From (3.3b), we observe that the steady-state oscillation frequency is determined by L_1 and C_s , in other words, X_1 and X_s respectively.
- Since the voltages at Port 1 and Port 2 are related, if oscillation occur at Port 1, then oscillation will also occur at Port 2.
- From this brief discussion, we use RC and RL networks for the source and amplifier input respectively, however we can distill the more general requirements for oscillation to start-up and achieve steady-state operation for series representation in terms of resistance and reactance:

$$R_s + R_1 |_{\omega_o} < 0 \quad (3.5a)$$

$$X_s + X_1 |_{\omega_o} = 0 \quad (3.5b)$$

Start-up

$$R_s + R_1 |_{\omega_o} = 0 \quad (3.6a)$$

$$X_s + X_1 |_{\omega_o} = 0 \quad (3.6b)$$

Steady-state


April 2012

© 2006 by Fabian Kung Wai Lee

27

Illustration of Oscillation Start-Up and Steady-State

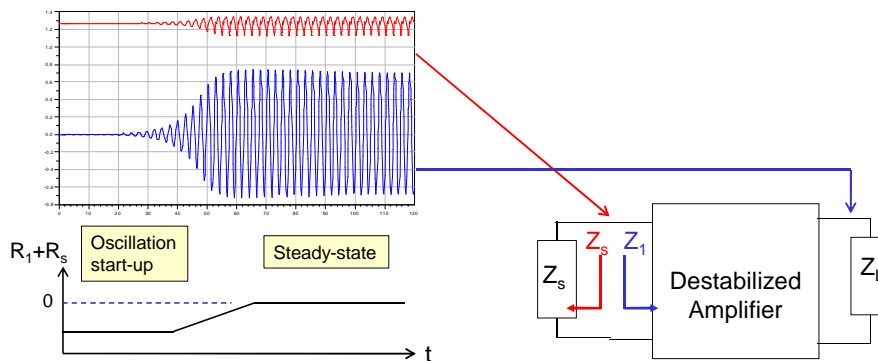- The oscillation start-up process and steady-state are illustrated.



We need to note that this is a very simplistic view of oscillators. Oscillators are autonomous non-linear dynamical systems, and the steady-state condition is a form of **Limit Cycles**.


April 2012

© 2006 by Fabian Kung Wai Lee

28

Summary of Oscillation Requirements Using Series Network

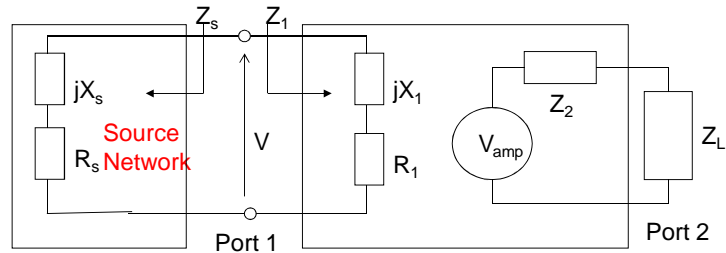- By expressing Z_s and Z_1 in terms of resistance and reactance, we conclude that the requirement for oscillation are.



$$R_s + R_1 |_{\omega_o} = 0$$

(3.6a)

$$X_s + X_1 |_{\omega_o} = 0$$

(3.6b)

Steady-state

$$R_s + R_1 |_{\omega_o} < 0$$

(3.5a)

$$X_s + X_1 |_{\omega_o} = 0$$

(3.5b)

Start-up

- A similar expression for Z_2 and Z_L can also be obtained, but we shall not be concerned with these here.

April 2012

© 2006 by Fabian Kung Wai Lee

29

The Resonator

- The source network Z_s is usually called the **Resonator**, as it is clear that equations (3.5b) and (3.6b) represent the resonance condition between the source network and the amplifier input.
- The design of the resonator is extremely important.
- We shall see later that an important parameter of the oscillator, the Phase Noise is dependent on the quality of the resonator.


April 2012

© 2006 by Fabian Kung Wai Lee

30

Summary of Oscillation Requirements Using Parallel Network

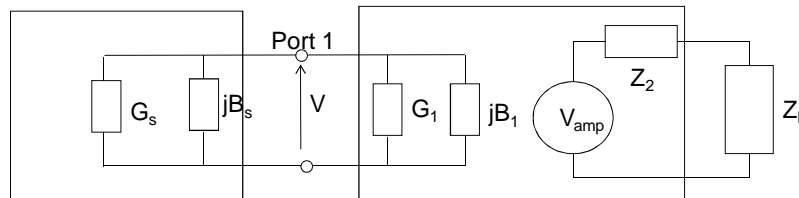- If we model the source network and input to the amplifier as parallel networks, the following dual of equations (3.5) and (3.6) are obtained.



- The start-up and steady-state conditions are:

$$G_s + G_1 |_{\omega_o} = 0 \quad (3.7a) \quad G_s + G_1 |_{\omega_o} < 0 \quad (3.8a)$$

$$B_s + B_1 |_{\omega_o} = 0 \quad (3.7b) \quad B_s + B_1 |_{\omega_o} = 0 \quad (3.8b)$$

Steady-state

Start-up

April 2012

© 2006 by Fabian Kung Wai Lee

31

Series or Parallel Representation? (1)

- The question is which to use? Series or parallel network representation? This is not an easy question to answer as the destabilized amplifier is operating in nonlinear region as oscillator.
- Concept of impedance is not valid and our discussion is only an approximation at best.
- We can assume series representation, and worked out the corresponding resonator impedance. If after computer simulation we discover that the actual oscillating frequency is far from our prediction (if there's any oscillation at all!), then it probably means that the series representation is incorrect, and we should try the parallel representation.
- Another clue to whether series or parallel representation is more accurate is to observe the current and voltage in the resonator. For series circuit the current is near sinusoidal, where as for parallel circuit it is the voltage that is sinusoidal.

April 2012

© 2006 by Fabian Kung Wai Lee

32

Series or Parallel Representation? (2)

- Reference [7] illustrates another effective alternative, by computing the **large-signal** S_{11} of Port 1 (with respect to Z_0) using CAD software.
- $1/S_{11}$ is then plotted on a Smith Chart as a function of input signal magnitude at the operating frequency.
- By comparing the locus of $1/S_{11}$ as input signal magnitude is gradually increased with the coordinate of constant X or constant B circles on the Smith Chart, we can decide whether series or parallel form approximates Port 1 best.
- We will adopt this approach, but plot S_{11} instead of $1/S_{11}$. This will be illustrated in the examples in next section.
- Do note that there are other reasons that can cause the actual oscillation frequency to deviate a lot from prediction, such as frequency stability issue (see [1] and [7]).

4.0 Fixed Frequency Negative Resistance Oscillator Design

Procedures of Designing Fixed Frequency Oscillator (1)

- **Step 1** - Design a transistor/FET amplifier circuit.
- **Step 2** - Make the circuit unstable by adding positive feedback at radio frequency, for instance, adding series inductor at the base for common-base configuration.
- **Step 3** - Determine the frequency of oscillation ω_0 and extract S-parameters at that frequency.
- **Step 4** – With the aid of Smith Chart and Load Stability Circle, make $R_1 < 0$ by selecting Γ_L in the unstable region.
- **Step 5 (Optional)** – Perform a large-signal analysis (e.g. Harmonic Balance analysis) and plot large-signal S_{11} versus input magnitude on Smith Chart. Decide whether series or parallel form to use.
- **Step 6** - Find $Z_1 = R_1 + jX_1$ (Assuming series form).

April 2012

© 2006 by Fabian Kung Wai Lee

35

Procedures of Designing Fixed Frequency Oscillator (2)

- **Step 7** – Find R_s and X_s so that $R_1 + R_s < 0$, $X_1 + X_s = 0$ at ω_0 . We can use the rule of thumb $R_s = (1/3)|R_1|$ to control the harmonics content at steady-state.
- **Step 8** - Design the impedance transformation network for Z_s and Z_L .
- **Step 9** - Built the circuit or run a computer simulation to verify that the circuit can indeed starts oscillating when power is connected.
- **Note:** Alternatively we may begin Step 4 using Source Stability Circle, select Γ_s in the unstable region so that R_2 or G_2 is negative at ω_0 .

April 2012

© 2006 by Fabian Kung Wai Lee

36

Making an Amplifier Unstable (1)

- An amplifier can be made unstable by providing some kind of local positive feedback.
- Two favorite transistor amplifier configurations used for oscillator design are the **Common-Base configuration with Base feedback** and **Common-Emitter configuration with Emitter degeneration**.


April 2012

© 2006 by Fabian Kung Wai Lee

37

Making an Amplifier Unstable (2)

This is a practical model of an inductor

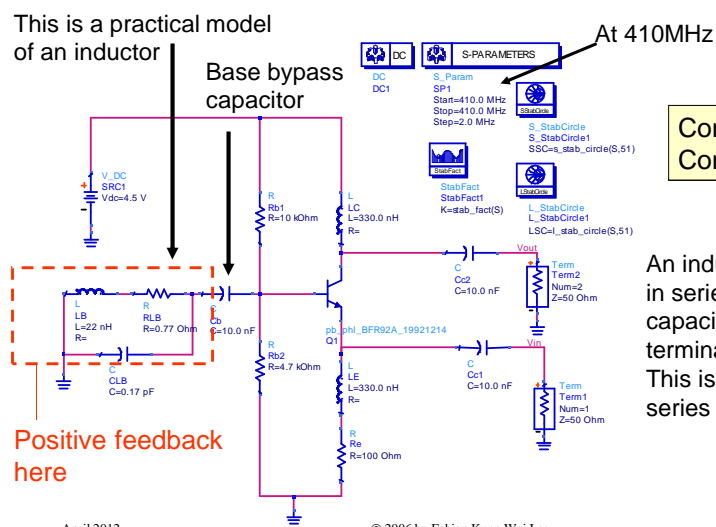

April 2012


© 2006 by Fabian Kung Wai Lee

38

Making an Amplifier Unstable (3)

freq	K			
410.0MHz	-0.987			
freq	S(1,1)	S(1,2)	S(2,1)	S(2,2)
410.0MHz	1.118 / 165.6...	0.162 / 166.9...	2.068 / -12.723	1.154 / -3.535

s₂₂ and s₁₁ have magnitude > 1

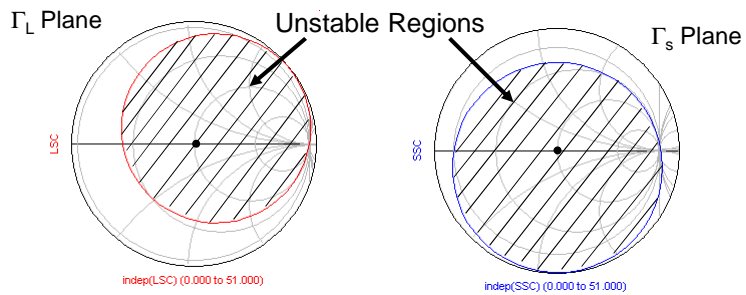


April 2012

© 2006 by Fabian Kung Wai Lee

39

Making an Amplifier Unstable (4)

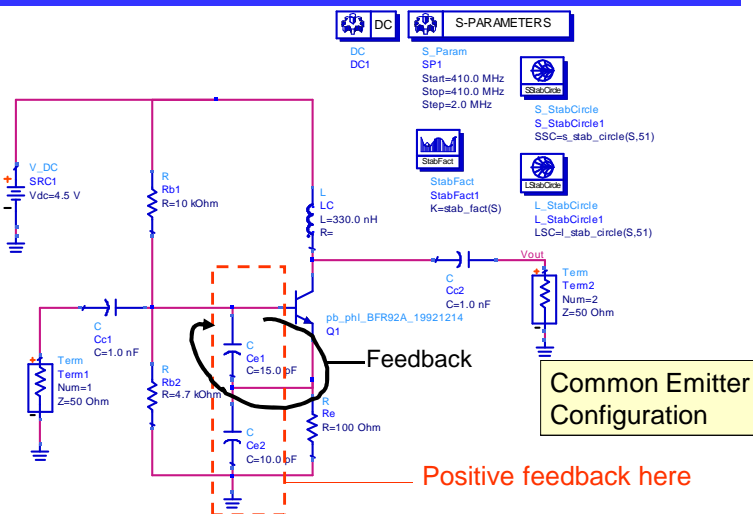

April 2012


© 2006 by Fabian Kung Wai Lee

40

Making an Amplifier Unstable (5)

S_{22} and S_{11} have magnitude > 1

freq	K			
410.0MHz	-0.516			
freq	S(1,1)	S(1,2)	S(2,1)	S(2,2)
410.0MHz	3.067 / -47.641	0.251 / 62.636	6.149 / 176.803	1.157 / -21.427

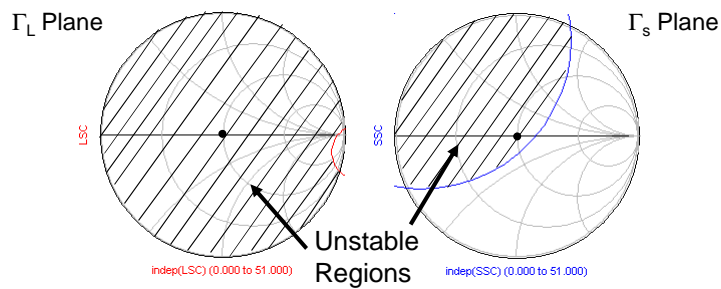


April 2012

© 2006 by Fabian Kung Wai Lee

41

Precautions

- The requirement $R_s = (1/3)|R_1|$ is a rule of thumb to provide the excess gain to start up oscillation.
- R_s that is too large (near $|R_1|$) runs the risk of oscillator fails to start up due to component characteristic deviation.
- While R_s that is too small (smaller than $(1/3)|R_1|$) causes too much non-linearity in the circuit, this will result in large harmonic distortion of the output waveform.

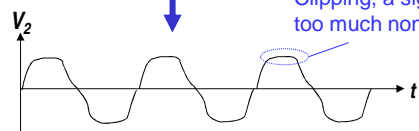

R_s too small

For more discussion about the $R_s = (1/3)|R_1|$ rule, and on the sufficient condition for oscillation, see [6], which list further requirements.



R_s too large

April 2012

© 2006 by Fabian Kung Wai Lee

42

Aid for Oscillator Design - Constant $|\Gamma_1|$ Circle (1)

- In choosing a suitable Γ_L to make $|\Gamma_L| > 1$, we would like to know the range of Γ_L that would result in a specific $|\Gamma_1|$.
- It turns out that if we fix $|\Gamma_1|$, the range of load reflection coefficient that result in this value falls on a circle in the Smith chart for Γ_L .
- The radius and center of this circle can be derived from:

$$\Gamma_1 = \frac{S_{11} - \Gamma_L D}{1 - S_{22} \Gamma_L}$$

- Assuming $\rho = |\Gamma_1|$:

By fixing $|\Gamma_1|$ and changing Γ_L .

$$T_{\text{center}} = \frac{-\rho^2 S_{22}^* + D^* S_{11}}{|D|^2 - \rho^2 |S_{22}|^2} \quad (4.1a)$$

$$\text{Radius} = \rho \frac{|S_{12} S_{21}|}{\left| |D|^2 - \rho^2 |S_{22}|^2 \right|} \quad (4.1b)$$

Aid for Oscillator Design - Constant $|\Gamma_1|$ Circle (2)

- The Constant $|\Gamma_1|$ Circle is extremely useful in helping us to choose a suitable load reflection coefficient. Usually we would choose Γ_L that would result in $|\Gamma_1| = 1.5$ or larger.
- Similarly Constant $|\Gamma_2|$ Circle can also be plotted for the source reflection coefficient. The expressions for center and radius is similar to the case for Constant $|\Gamma_1|$ Circle except we interchange s_{11} and s_{22} , Γ_L and Γ_s . See Ref [1] and [2] for details of derivation.

Example 4.1 – CB Fixed Frequency Oscillator Design

- In this example, the design of a fixed frequency oscillator operating at 410MHz will be demonstrated using BFR92A transistor in SOT23 package. The transistor will be biased in Common-Base configuration.
- It is assumed that a 50Ω load will be connected to the output of the oscillator. The schematic of the basic amplifier circuit is as shown in the following slide.
- The design is performed using Agilent's ADS software, but the author would like to stress that virtually any RF CAD package is suitable for this exercise.


April 2012

© 2006 by Fabian Kung Wai Lee

45

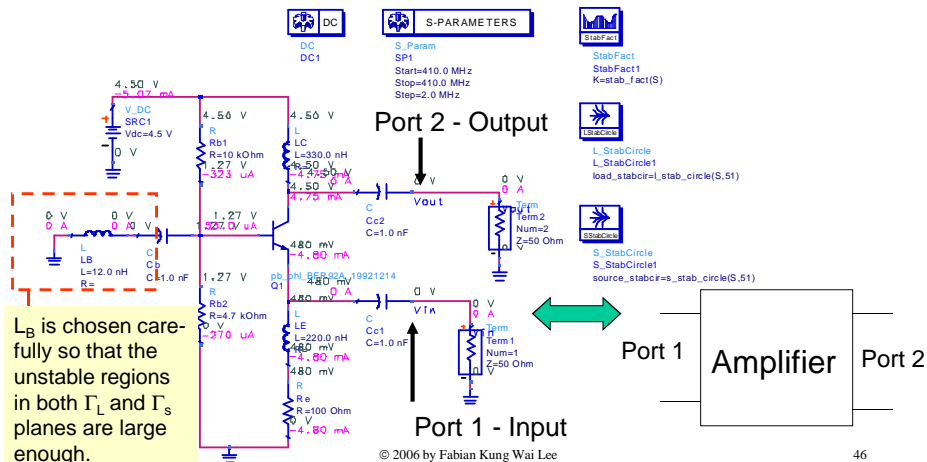Example 4.1 Cont...


- Step 1 and 2 - DC biasing circuit design and S-parameter extraction.



46

Example 4.1 Cont...

freq	K			
410.0MHz	-0.987			
freq	S(1,1)	S(1,2)	S(2,1)	S(2,2)
410.0MHz	1.118 / 165.6...	0.162 / 166.9...	2.068 / -12.723	1.154 / -3.535

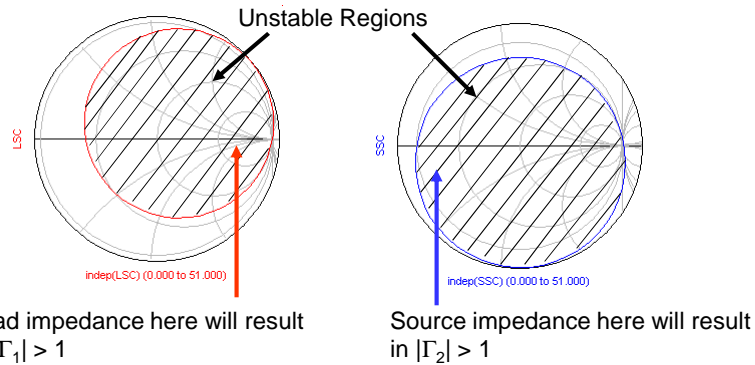


April 2012

© 2006 by Fabian Kung Wai Lee

47

Example 4.1 Cont...

- **Step 3 and 4** - Choosing suitable Γ_L that cause $|\Gamma_1| > 1$ at 410MHz. We plot a few constant $|\Gamma_1|$ circles on the Γ_L plane to assist us in choosing a suitable load reflection coefficient.

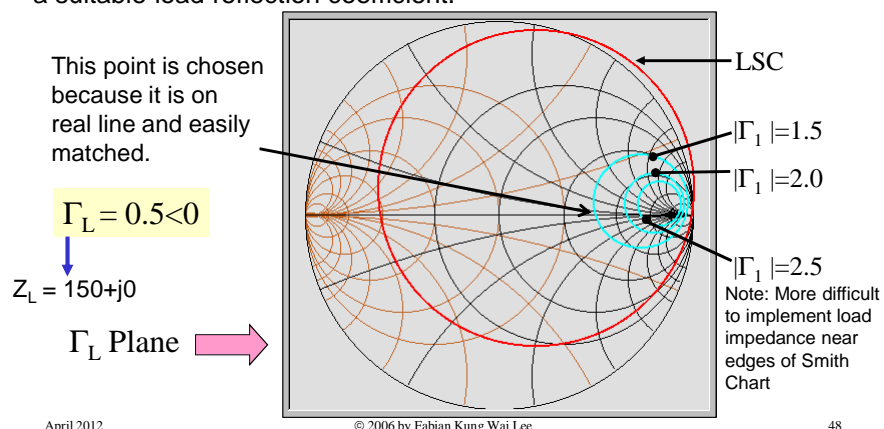

April 2012

© 2006 by Fabian Kung Wai Lee

48

Example 4.1 Cont...

Extra

- Step 5** – To check whether the input of the destabilized amplifier is closer to series or parallel form. We perform large-signal analysis and observe the S_{11} at the input of the destabilized amplifier.

Large-signal S-parameter Analysis control in ADS software.

We are measuring large-signal S_{11} looking towards here

April 2012 © 2006 by Fabian Kung Wai Lee 49

Example 4.1 Cont...

Extra

- Compare the locus of S_{11} and the constant X and constant B circles on the Smith Chart, it is clear the locus is more parallel to the constant X circle. Also the direction of S_{11} is moving from negative R to positive R as input power level is increased. We conclude the **Series form** is more appropriate.

Direction of S_{11} as magnitude of P_{1tone} source is increased

Locus of S_{11} versus P_{1tone} power at 410MHz (from -20 to -5 dBm)

Compare

Region where R_1 or G_1 is negative

Boundary of Normal Smith Chart

Region where R_1 or G_1 is positive

Poutv (-20.000 to -5.000)

April 2012 © 2006 by Fabian Kung Wai Lee 50

Example 4.1 Cont...

- **Step 6** – Using the series form, we find the small-signal input impedance Z_1 at 410MHz. So the resonator would also be a series network.
- For $Z_L = 150$ or $\Gamma_L = 0.5 < 0$:

$$\Gamma_1 = \frac{S_{11} - D\Gamma_L}{1 - S_{22}\Gamma_L} = -1.422 + j0.479$$

$$Z_1 = Z_o \frac{1 + \Gamma_1}{1 - \Gamma_1} = -10.257 + j7.851$$

\uparrow R_1 \downarrow X_1

- **Step 7** - Finding the suitable source impedance to fulfill $R_1 + R_s < 0$, $X_1 + X_s = 0$:

$$R_s = \frac{1}{3} |R_1| \cong 3.42$$

$$X_s = -X_1 \cong -7.851$$


April 2012

© 2006 by Fabian Kung Wai Lee

51

Example 4.1 Cont...

- The system block diagram:

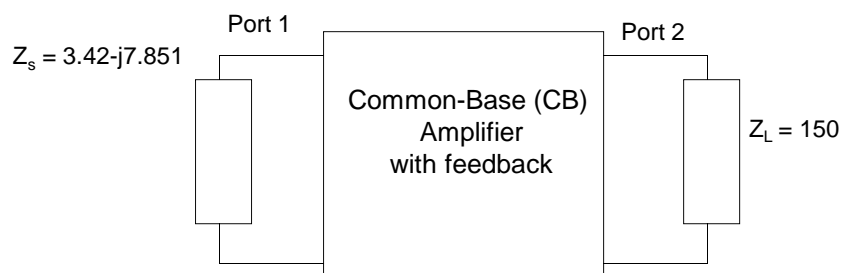


April 2012

© 2006 by Fabian Kung Wai Lee


52

Example 4.1 Cont...

- **Step 5** - Realization of the source and load impedance at 410MHz.

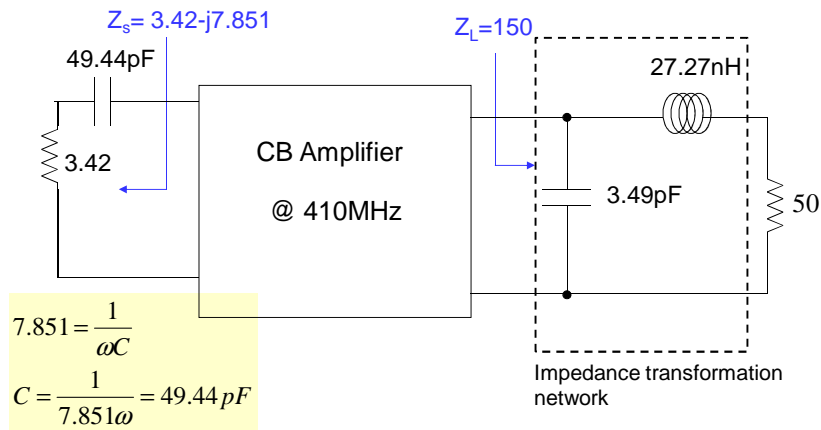


Example 4.1 Cont... - Verification Thru Simulation

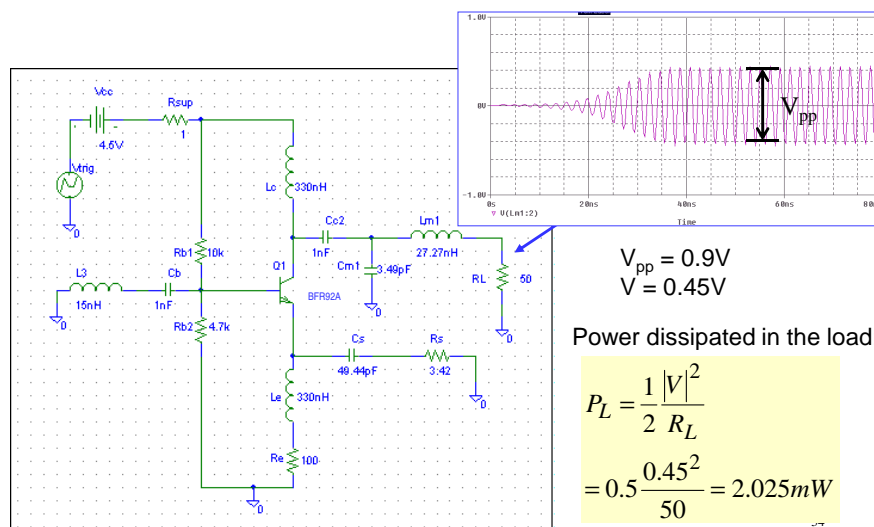

Example 4.1 Cont... - Verification Thru Simulation

- Performing Fourier Analysis on the steady state wave form:

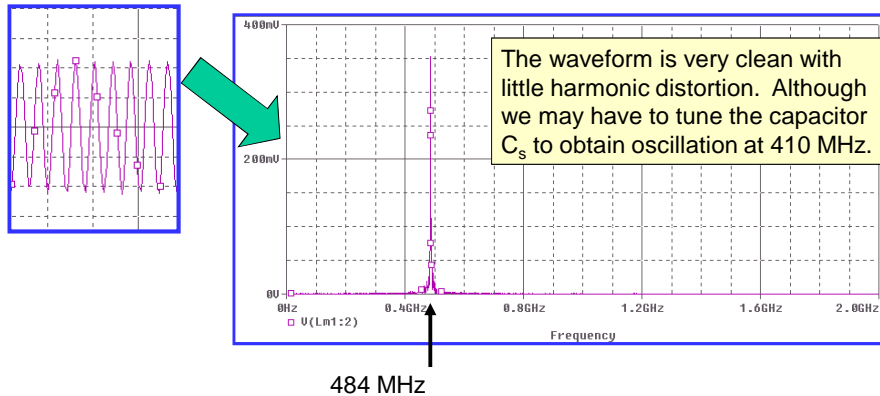


April 2012

© 2006 by Fabian Kung Wai Lee

55

Example 4.1 Cont... – The Prototype

Voltage at the base terminal and 50 Ohms load resistor of the fixed frequency oscillator:

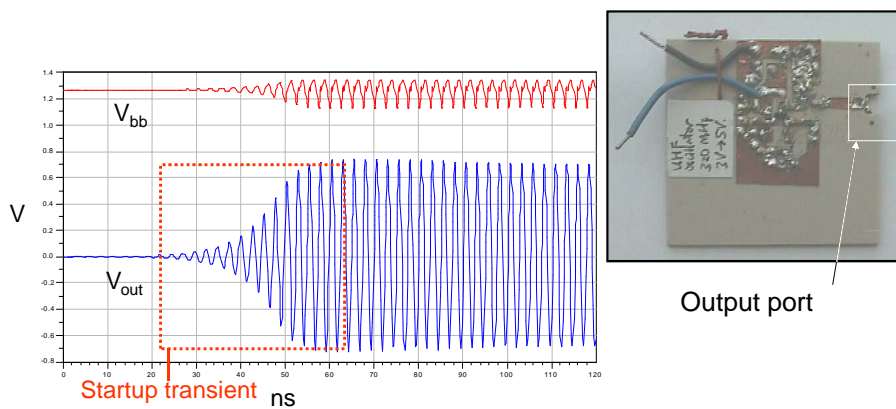


April 2012

© 2006 by Fabian Kung Wai Lee

56


Example 4.2 – 450 MHz CE Fixed Frequency Oscillator Design

- Small-signal AC or S-parameter analysis, to show that R_1 or G_1 is negative at the intended oscillation frequency of 450 MHz.

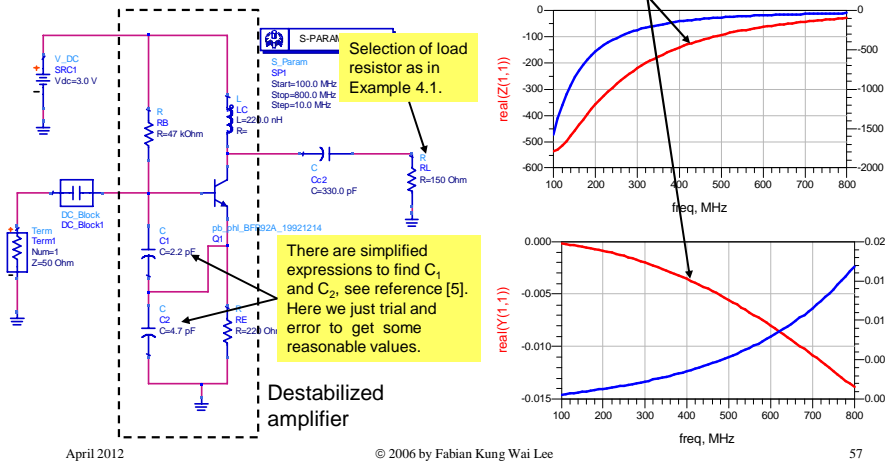


Example 4.2 Cont...

- The large-signal analysis to check for suitable representation.

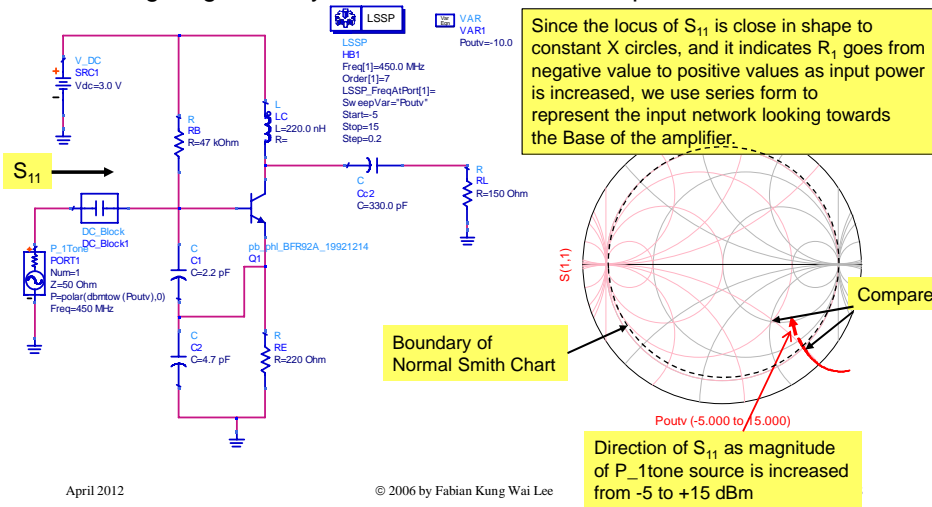


Example 4.2 Cont...

- Using a series RL for the resonator, and performing time-domain simulation to verify that the circuit will oscillate.

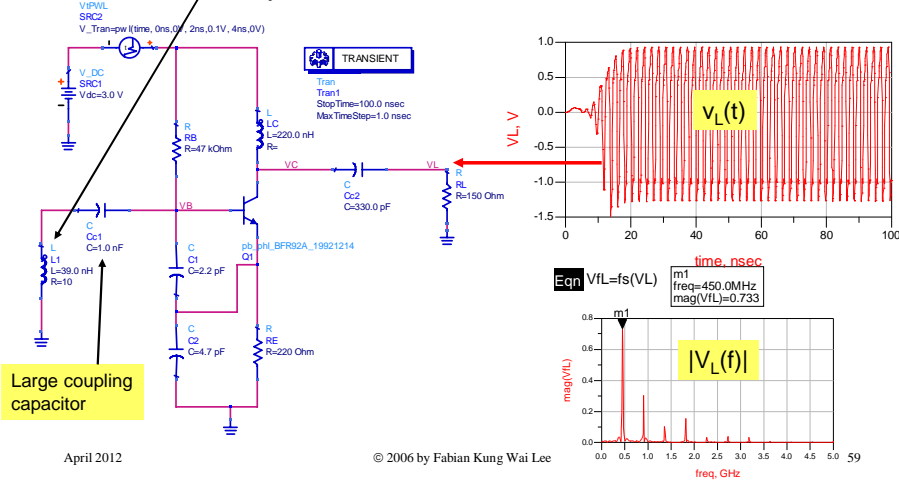

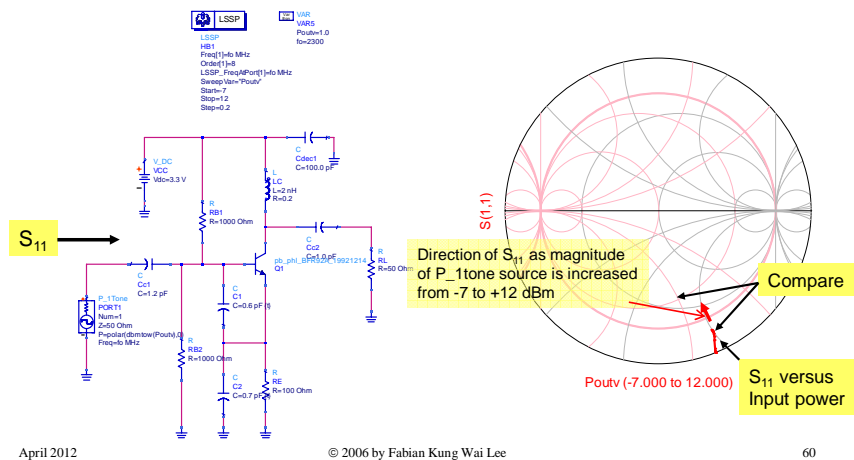Example 4.3 – Parallel Representation

- An example where the network looking into the Base of the destabilized amplifier is more appropriate as parallel RC network.



Frequency Stability

- The process of oscillation depends on the non-linear behavior of the negative-resistance network.
- The conditions discussed, e.g. equations (3.1), (3.8), (3.9), (3.10) and (3.11) are not enough to guarantee a stable state of oscillation. In particular, stability requires that any perturbation in current, voltage and frequency will be damped out, allowing the oscillator to return to its initial state.
- The stability of oscillation can be expressed in terms of the partial derivative of the sum $Z_{in} + Z_s$ or $Y_{in} + Y_s$ of the input port (or output port).
- The discussion is beyond the scope of this chapter for now, and the reader should refer to [1] and [7] for the concepts.

Some Steps to Improve Oscillator Performance

- To improve the frequency stability of the oscillator, the following steps can be taken.
- Use components with known temperature coefficients, especially capacitors.
- Neutralize, or swamp-out with resistors, the effects of active device variations due to temperature, power supply and circuit load changes.
- Operate the oscillator on lower power.
- Reduce noise, use shielding, AGC (automatic gain control) and bias-line filtering.
- Use an oven or temperature compensating circuitry (such as thermistor).
- Use differential oscillator architecture (see [4] and [7]).

Extra References for This Section

- Some recommended journal papers on frequency stability of oscillator:
- Kurokawa K., "Some basic characteristics of broadband negative resistance oscillator circuits", Bell System Technical Journal, pp. 1937-1955, 1969.
- Nguyen N.M., Meyer R.G., "Start-up and frequency stability in high-frequency oscillators", IEEE journal of Solid-State Circuits, vol 27, no. 5 pp.810-819, 1992.
- Grebennikov A. V., "Stability of negative resistance oscillator circuits", International journal of Electronic Engineering Education, Vol. 36, pp. 242-254, 1999.

April 2012


© 2006 by Fabian Kung Wai Lee

63

Reconciliation Between Feedback and Negative Resistance Oscillator Perspectives

Extra

- It must be emphasized that the circuit we obtained using negative resistance approach can be cast into the familiar feedback form. For instance an oscillator circuit similar to Example 4.2 can be redrawn as:

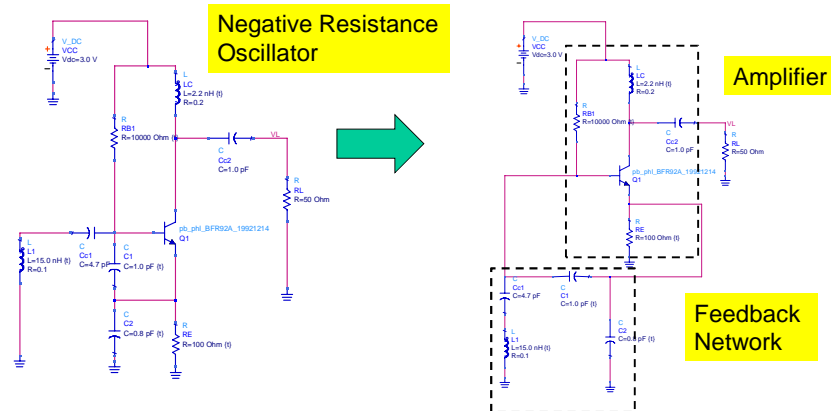

April 2012

© 2006 by Fabian Kung Wai Lee

64

5.0 Voltage Controlled Oscillator

April 2012

© 2006 by Fabian Kung Wai Lee

65

About the Voltage Controlled Oscillator (VCO) (1)

- A simple transistor VCO using Clapp-Gouriet or CE configuration will be designed to illustrate the principles of VCO.
- The transistor chosen for the job is BFR92A, a wide-band NPN transistor which comes in SOT-23 package.
- Similar concepts as in the design of fixed-frequency oscillators are employed. Where we design the biasing of the transistor, destabilize the network and carefully choose a load so that from the input port (Port 1), the oscillator circuit has an impedance (assuming series representation is valid):

$$Z_1(\omega) = R_1(\omega) + jX_1(\omega)$$

- Of which R_1 is negative, for a range of frequencies from ω_1 to ω_2 .

Lower


Upper

April 2012

© 2006 by Fabian Kung Wai Lee

66

About the Voltage Controlled Oscillator (VCO) (2)

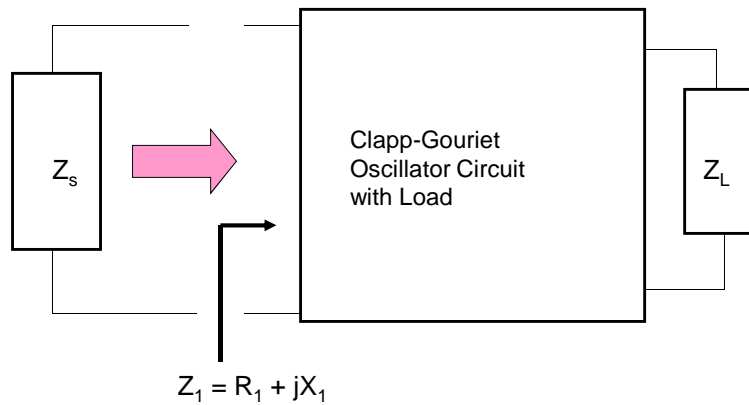

April 2012

© 2006 by Fabian Kung Wai Lee

67

About the Voltage Controlled Oscillator (VCO) (3)

- If we can connect a source impedance Z_s to the input port, such that within a range of frequencies from ω_1 to ω_2 :

$$Z_s(\omega) = R_s(\omega) + jX_s(\omega)$$

$$R_s(\omega) < |R_1(\omega)| \quad R_1(\omega) < 0 \quad X_s(\omega) = X_1(\omega)$$

- The circuit will oscillate within this range of frequencies. By changing the value of X_s , one can change the oscillation frequency.

The rationale is that only the initial spectral of the noise signal fulfilling $X_s = X_1$ will start the oscillation.

- For example, if X_1 is positive, then X_s must be negative, and it can be generated by a series capacitor. By changing the capacitance, one can change the oscillation frequency of the circuit.
- If X_1 is negative, X_s must be positive. A variable capacitor in series with a suitable inductor will allow us to adjust the value of X_s .

April 2012


© 2006 by Fabian Kung Wai Lee

68

Schematic of the VCO

Initial noise source to start the oscillation

Variable capacitance tuning network

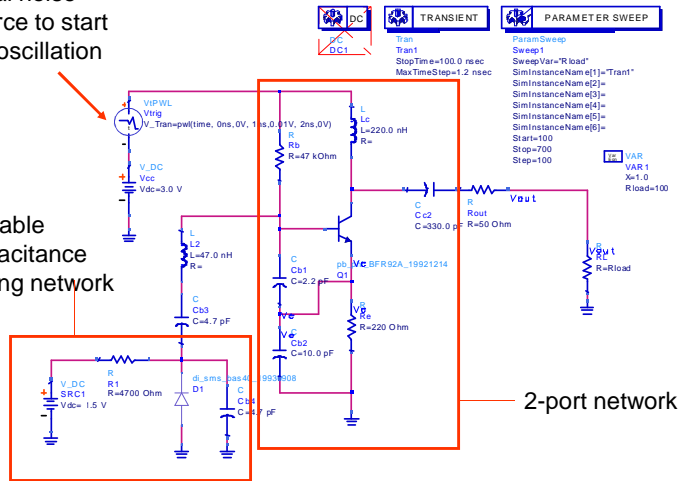

More on the Schematic


- L_2 together with C_{b3} , C_{b4} and the junction capacitance of D_1 can produce a range of reactance value, from negative to positive. Together these components form the **frequency determining network**.
- C_{b4} is optional, it is used to introduce a capacitive offset to the junction capacitance of D_1 .
- R_1 is used to isolate the control voltage V_{dc} from the frequency determining network. It must be a high quality SMD resistor. The effectiveness of isolation can be improved by adding a RF choke in series with R_1 and a shunt capacitor at the control voltage.
- Notice that the frequency determining network has no actual resistance to counter the effect of $|R_1(\omega)|$. This is provided by the loss resistance of L_2 and the junction resistance of D_1 .

April 2012

© 2006 by Fabian Kung Wai Lee

70

Time Domain Result

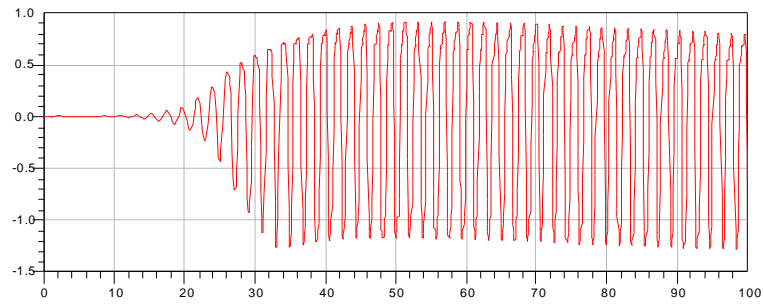

V_{out} when $V_{dc} = -1.5V$


April 2012

© 2006 by Fabian Kung Wai Lee

71

Load-Pull Experiment

- Peak-to-peak output voltage versus R_{load} for $V_{dc} = -1.5V$.

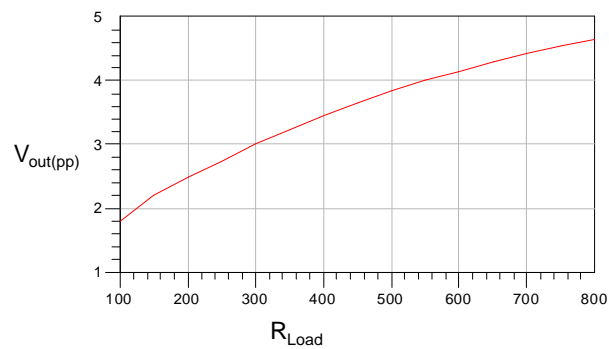


April 2012

© 2006 by Fabian Kung Wai Lee

72

Controlling Harmonic Distortion (1)

- Since the resistance in the frequency determining network is too small, large amount of non-linearity is needed to limit the output voltage waveform, as shown below there is a lot of distortion.

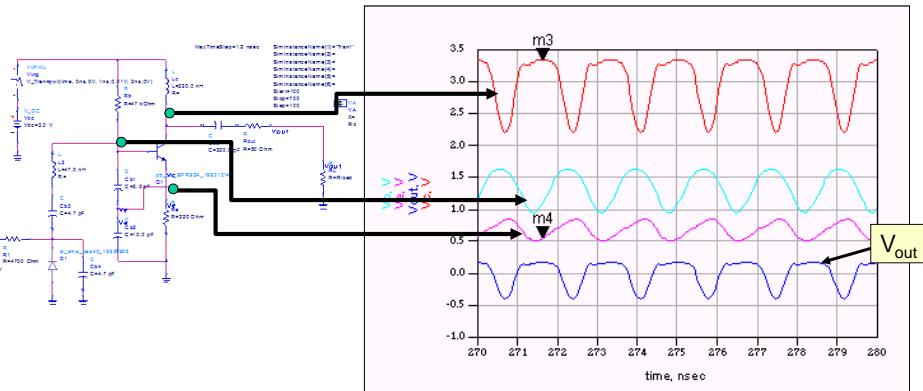

April 2012

© 2006 by Fabian Kung Wai Lee

73

Controlling Harmonic Distortion (2)

- The distortion generates substantial amount of higher harmonics.
- This can be reduced by decreasing the positive feedback, by adding a small capacitance across the collector and base of transistor Q_1 . This is shown in the next slide.

April 2012


© 2006 by Fabian Kung Wai Lee

74

Controlling Harmonic Distortion (3)

The observant person would probably notice that we can also reduce the harmonic distortion by introducing a series resistance in the tuning network. However this is not advisable as the phase noise at the oscillator's output will increase (more about this later).

Capacitor to control positive feedback

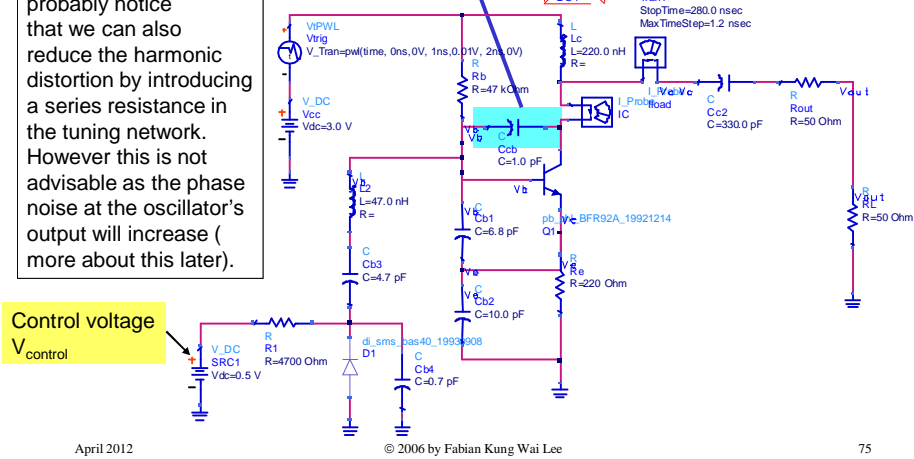


April 2012

© 2006 by Fabian Kung Wai Lee

75

Controlling Harmonic Distortion (4)

- The output waveform V_{out} after this modification is shown below:

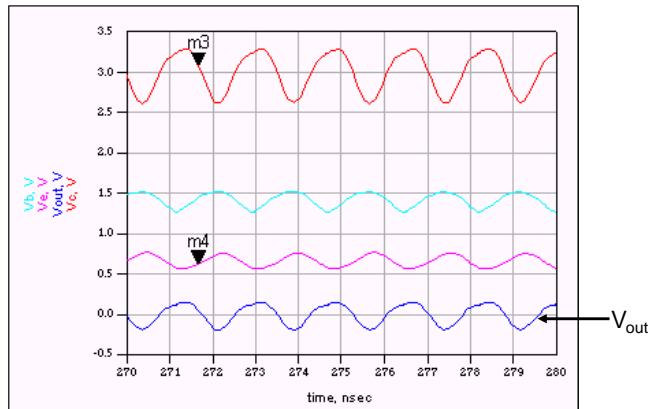

April 2012

© 2006 by Fabian Kung Wai Lee

76

Controlling Harmonic Distortion (5)

- Finally, it should be noted that we should also add a low-pass filter (LPF) at the output of the oscillator to suppress the higher harmonic components. Such LPF is usually called [Harmonic Filter](#).
- Since the oscillator is operating in nonlinear mode, care must be taken in designing the LPF.
- Another practical design example will illustrate this approach.

April 2012


© 2006 by Fabian Kung Wai Lee

77

The Tuning Range

- Actual measurement is carried out, with the frequency measured using a high bandwidth digital storage oscilloscope.

D_1 is BB149A,
a varactor
manufactured by
Phillips
Semiconductor (Now
NXP).

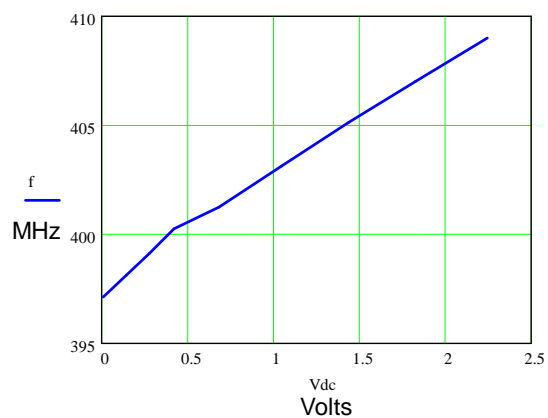

April 2012

© 2006 by Fabian Kung Wai Lee

78


Phase Noise in Oscillator (1)

Extra

- Since the oscillator output is periodic. In frequency domain we would expect a series of harmonics.
- In a practical oscillation system, the instantaneous frequency and magnitude of oscillation are not constant. These will fluctuate as a function of time.

$$v_{osc}(t) = (V_o + m_{noise}(t)) \cos(\omega t + \theta + \theta_{noise}(t))$$

- These random fluctuations are noise, and in frequency domain the effect of the spectra will 'smear out'.

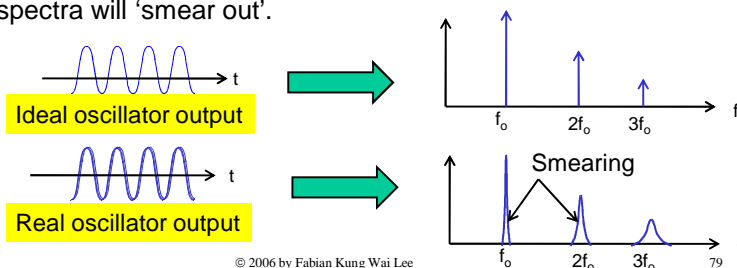


April 2012

© 2006 by Fabian Kung Wai Lee

Phase Noise in Oscillator (2)

Extra

- Mathematically, we can say that the instantaneous frequency and magnitude of oscillation are not constant. These will fluctuate as a function of time.
- As a result, the output in the frequency domain is 'smeared' out.

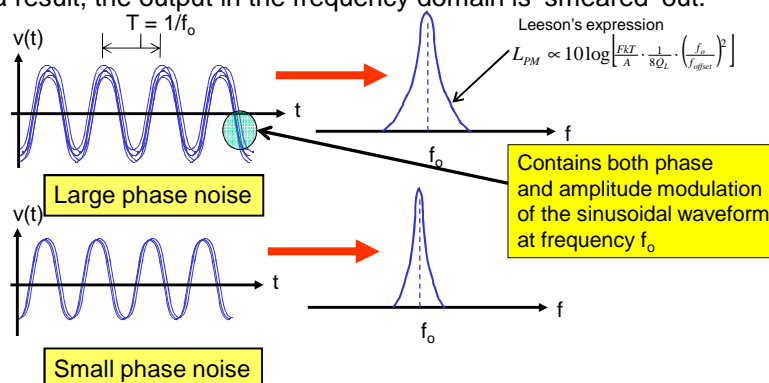

April 2012


© 2006 by Fabian Kung Wai Lee

80

Phase Noise in Oscillator (3)

Extra

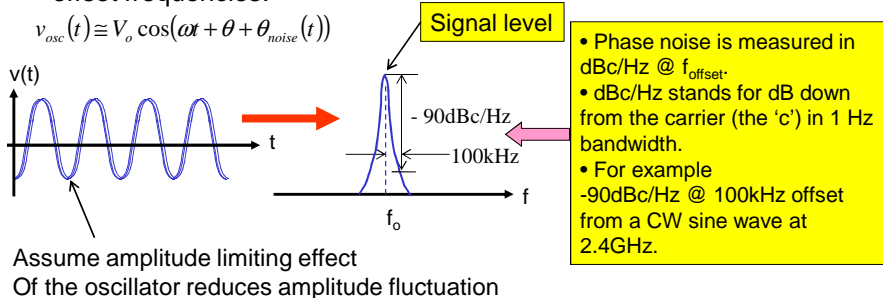
- Typically the magnitude fluctuation is small (or can be minimized) due to the oscillator nonlinear limiting process under steady-state.
- Thus the smearing is largely attributed to phase variation and is known as Phase Noise.
- Phase noise is measured with respect to the signal level at various offset frequencies.



Reducing Phase Noise (1)

Extra

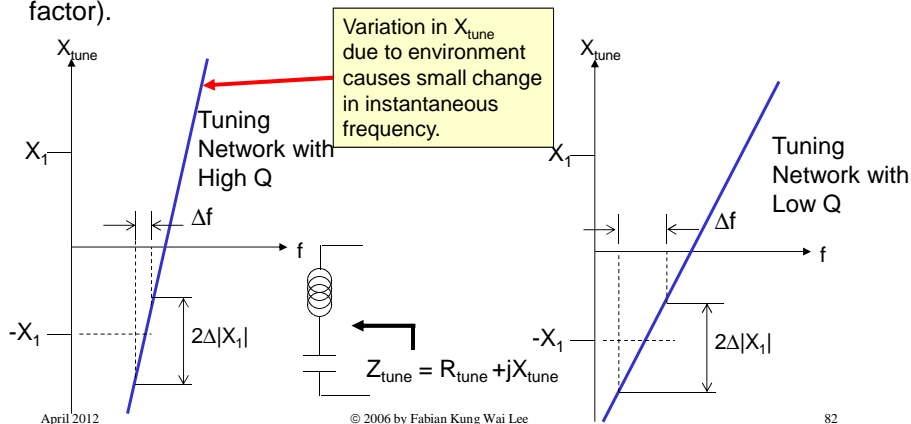- **Requirement 1:** The resonator network of an oscillator must have a high Q factor. This is an indication of low dissipation loss in the tuning network (See Chapter 3a – impedance transformation network on Q factor).





Reducing Phase Noise (2)

- A Q factor in the tuning network of at least 20 is needed for medium performance oscillator circuits at UHF. For highly stable oscillator, Q factor of the tuning network must be in excess of 1000.
- We have looked at LC tuning networks, which can give Q factor of up to 40. Ceramic resonator can provide Q factor greater than 500, while piezoelectric crystal can provide Q factor > 10000.
- At microwave frequency, the LC tuning networks can be substituted with transmission line sections.
- See R. W. Rhea, "Oscillator design & computer simulation", 2nd edition 1995, McGraw-Hill, or the book by R.E. Collin for more discussions on Q factor.
- **Requirement 2:** The power supply to the oscillator circuit should also be very stable to prevent unwanted amplitude modulation at the oscillator's output.

April 2012

© 2006 by Fabian Kung Wai Lee

83



Reducing Phase Noise (3)

- **Requirement 3:** The voltage level of V_{control} should be stable.
- **Requirement 4:** The circuit has to be properly shielded from electromagnetic interference from other modules.
- **Requirement 5:** Use low noise components in the construction of the oscillator, e.g. small resistance values, low-loss capacitors and inductors, low-loss PCB dielectric, use discrete components instead of integrated circuits.


April 2012

© 2006 by Fabian Kung Wai Lee

84

Extra Example of Phase Noise from VCOs

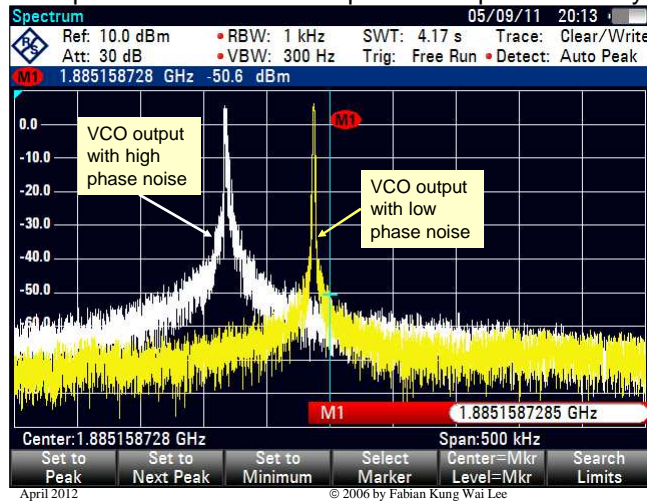- Comparison of two VCO outputs on a spectrum analyzer*.



*The spectrum analyzer internal oscillator must of course have a phase noise of an order of magnitude lower than our VCO under test.

85

Extra More Materials

- This short discussion cannot do justice to the material on phase noise.
- For instance the mathematical model of phase noise in oscillator and the famous Leeson's equation is not shown here. You can find further discussion in [4], and some material for further readings on this topic:
 - D. Schere, "The art of phase noise measurement", Hewlett Packard RF & Microwave Measurement Symposium, 1985.
 - T. Lee, A. Hajimiri, "The design of low noise oscillators", Kluwer, 1999.

April 2012


© 2006 by Fabian Kung Wai Lee

86



More on Varactor

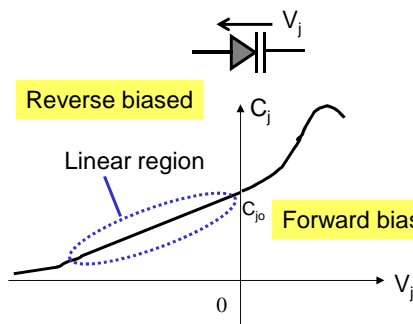- The varactor diode is basically a PN junction optimized for its linear junction capacitance.
- It is **always** operated in the reverse-biased mode to prevent nonlinearity, which generate harmonics.



- As we **increase** the negative biasing voltage V_j , C_j decreases, hence the oscillation frequency **increases**.
- The **abrupt junction** varactor has high Q, but low sensitivity (e.g. C_j varies little over large voltage change).
- The hyperabrupt junction varactor has low Q, but higher sensitivity.

April 2012

© 2006 by Fabian Kung Wai Lee


87



A Better Variable Capacitor Network

- The back-to-back varactors are commonly employed in a VCO circuit, so that at low $V_{control}$, when one of the diode is being affected by the AC voltage, the other is still being reverse biased.
- When a diode is forward biased, the PN junction capacitance becomes nonlinear.
- The reverse biased diode has smaller junction capacitance, and this dominates the overall capacitance of the back-to-back varactor network.
- This configuration helps to decrease the harmonic distortion.

At any one time, at least one of the diode will be reverse biased. The junction capacitance of the reverse biased diode will dominate the overall capacitance of the network.

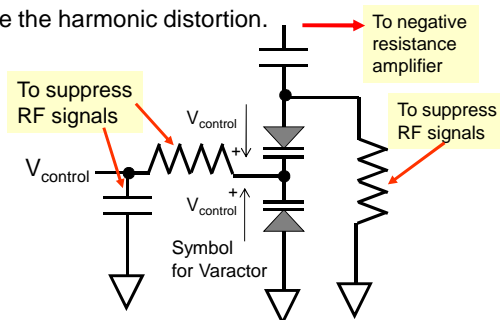

Sep 2013

© 2006 by Fabian Kung Wai Lee

88

Example 5.1 – VCO Design for Frequency Synthesizer

- To design a low power VCO that works from 810 MHz to 910 MHz.
- Power supply = 3.0V.
- Output power (into 50Ω load) minimum -3.0 dBm.


April 2012

© 2006 by Fabian Kung Wai Lee

89

Example 5.1 Cont...

- Checking the d.c. biasing and AC simulation.

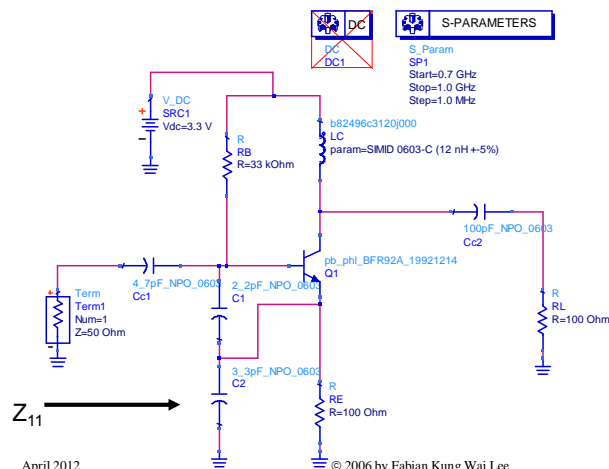


April 2012

© 2006 by Fabian Kung Wai Lee

90

Example 5.1 Cont...

- Checking the results – real and imaginary portion of Z_1 when output is terminated with $Z_L = 100\Omega$.

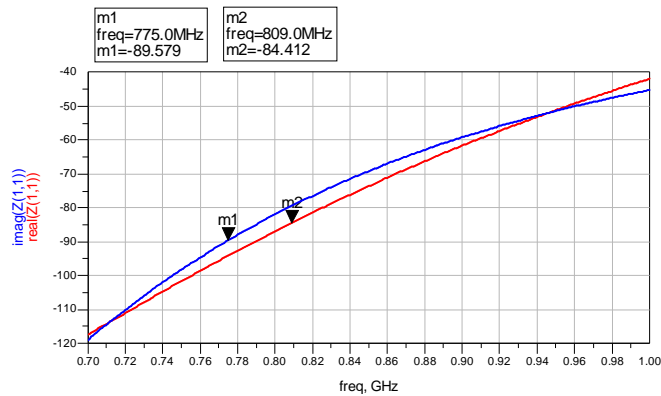


April 2012

© 2006 by Fabian Kung Wai Lee

91

Example 5.1 Cont...

- The resonator design.

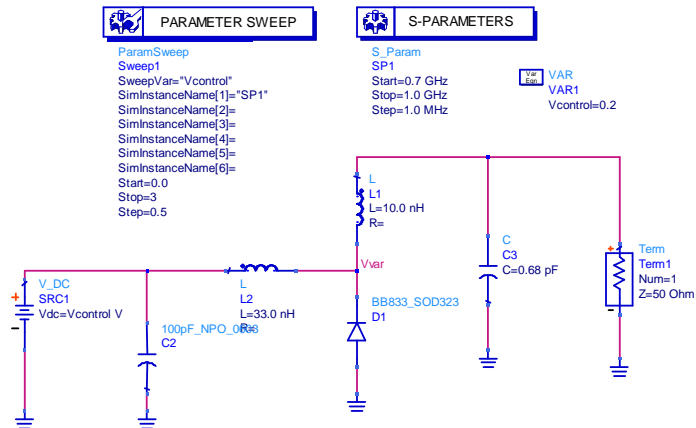


April 2012

© 2006 by Fabian Kung Wai Lee

92

Example 5.1 Cont...

- The resonator reactance.

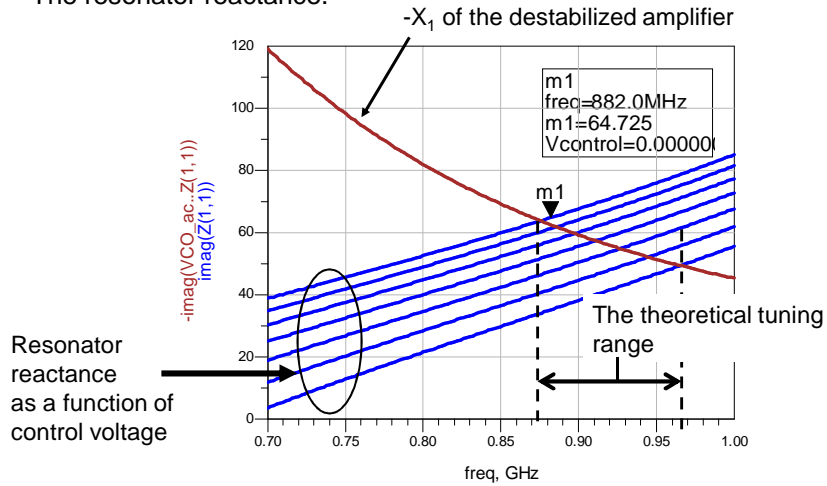


April 2012

© 2006 by Fabian Kung Wai Lee

93

Example 5.1 Cont...

- The complete schematic with the harmonic suppression filter.

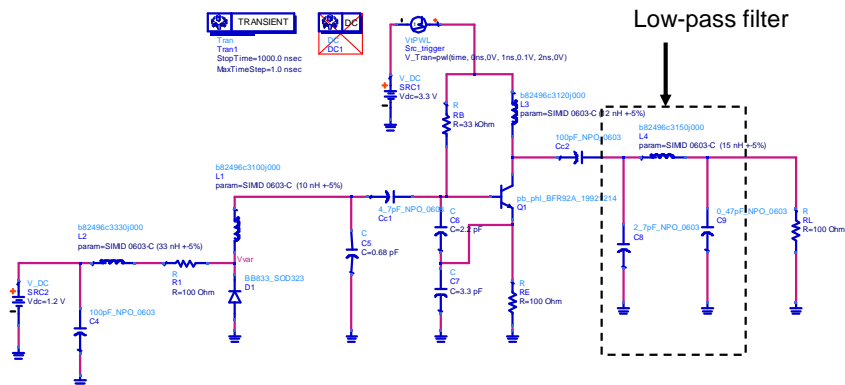



April 2012

© 2006 by Fabian Kung Wai Lee

94

Example 5.1 Cont...

- The prototype and the result captured from a spectrum analyzer (9 kHz to 3 GHz).

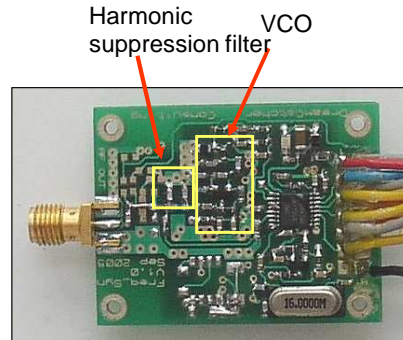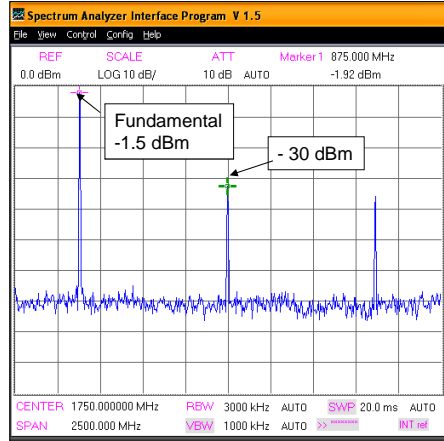


April 2012

© 2006 by Fabian Kung Wai Lee

95

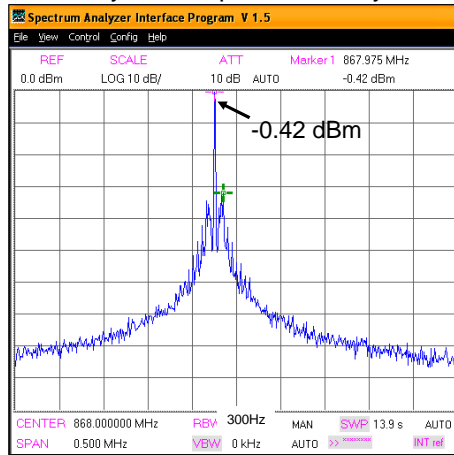Example 5.1 Cont...

- Examining the phase noise of the oscillator (of course the accuracy is limited by the stability of the spectrum analyzer used).



Span = 500 kHz
RBW = 300 Hz
VBW = 300 Hz


April 2012

© 2006 by Fabian Kung Wai Lee

96

Example 5.1 Cont...

- VCO gain (k_o) measurement setup:

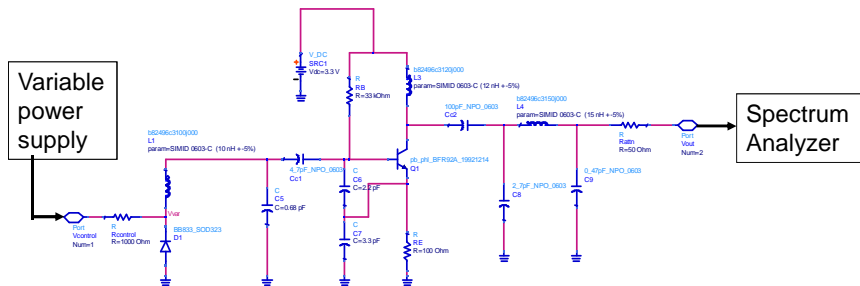


April 2012

© 2006 by Fabian Kung Wai Lee

97

Example 5.1 Cont...

- Measured results:

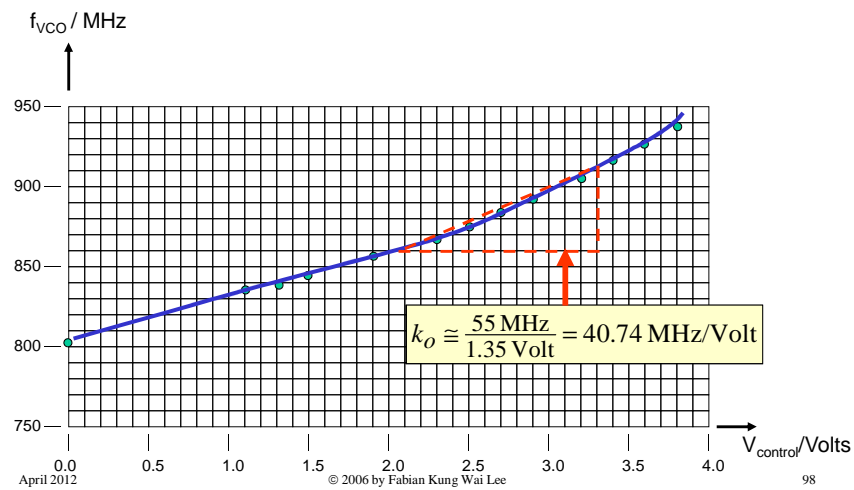

April 2012

© 2006 by Fabian Kung Wai Lee

98